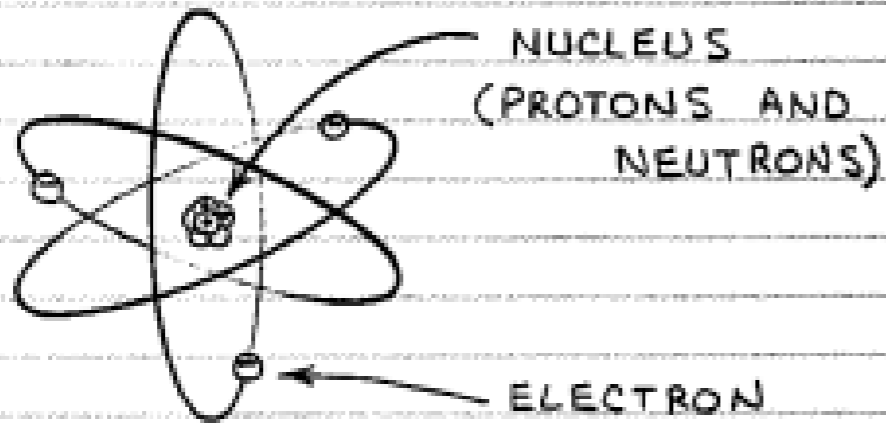





waag society

institute for art, science and technology


Principles of Electronics



LITHIUM ATOM

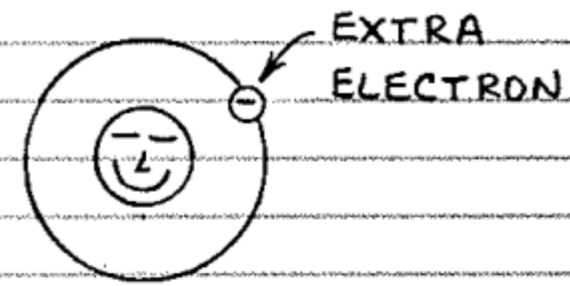

NEGATIVE ION

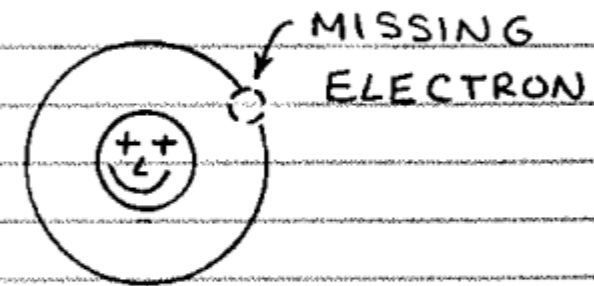

POSITIVE ION





A circuit

What is a circuit?

It's a **CLOSED LOOP** that electrons can travel in.

Electrons flow = Current

How can I generate a current?

The simplest circuit is

BATTERY + RESISTOR





Battery

The battery is the power supply of our circuit.



It has two sides:

+ / plus: VCC, V+, +V

- / minus: GND

Unit of measure: Volt (V).

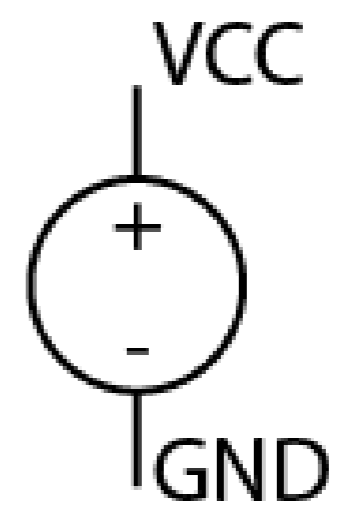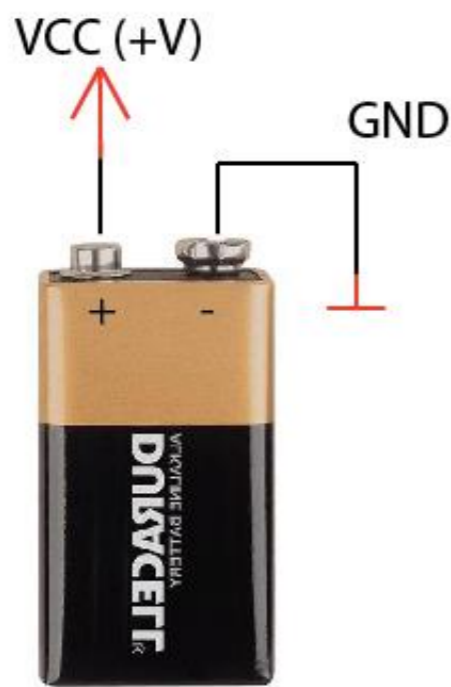Voltage:
It's the
difference
between two
points





Batteries & power supplies

VCC = 9V



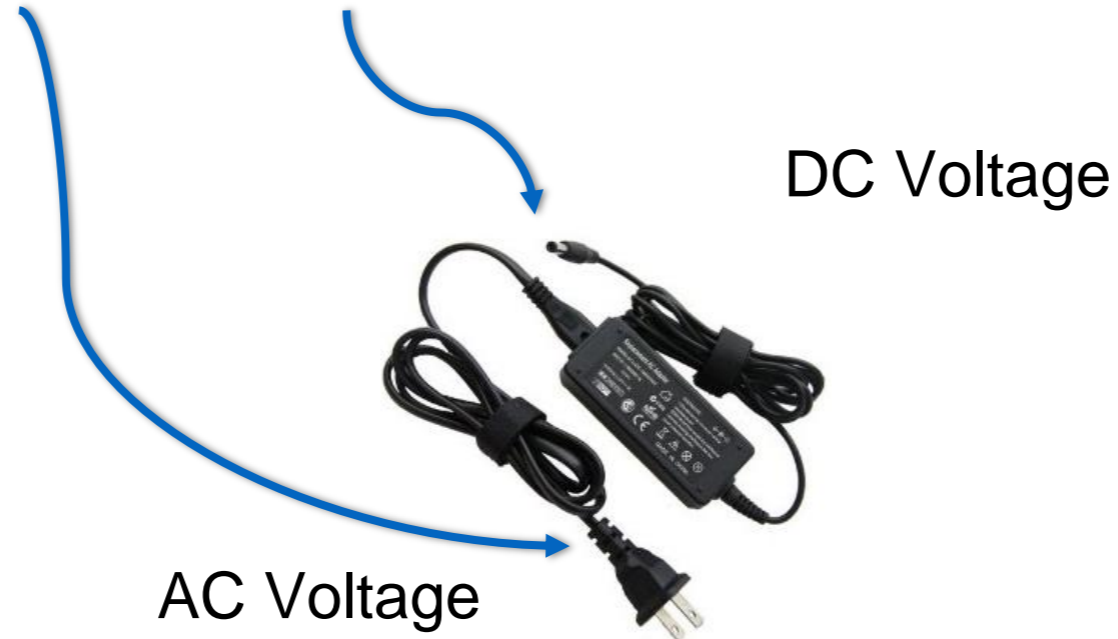
1.5V



3V



From the grid (220V) to 12V (the output that be different), VCC = 12V.



AC

DC



Resistor


It has two sides, it doesn't matter the orientation.

Unit of measure: Ohm (Ω).





The simplest circuit

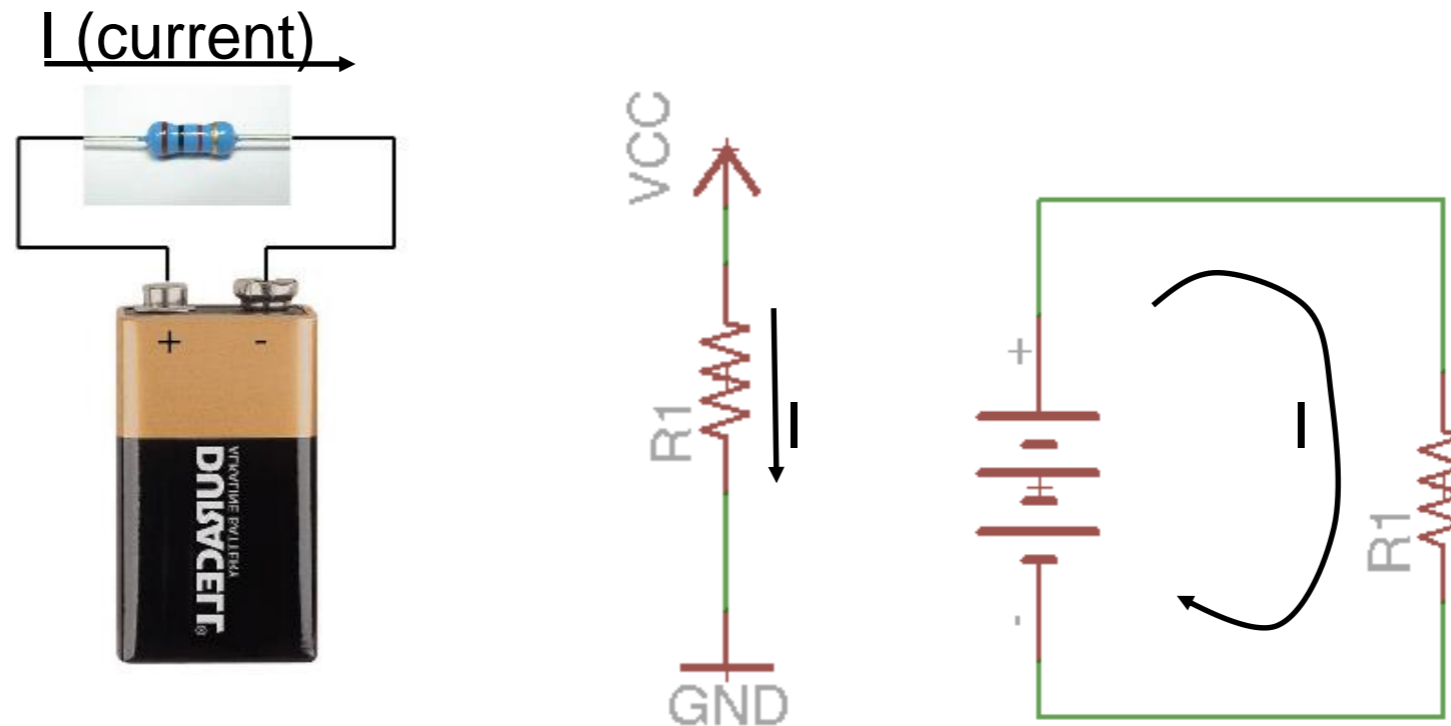

Voltage: is the difference in charge between two points.

Current: is the rate at which charge is flowing.


Resistance: is a material's tendency to resist the flow of charge (current).





1) No Slope = No Motion



2) Slope = Motion without control

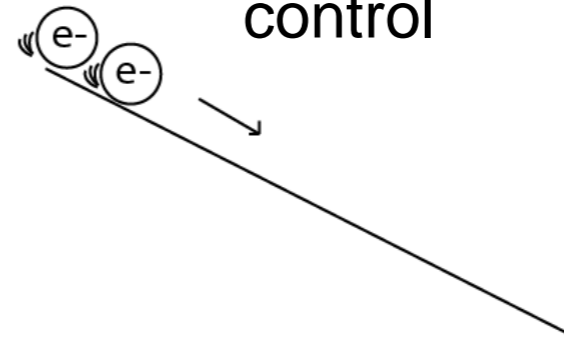


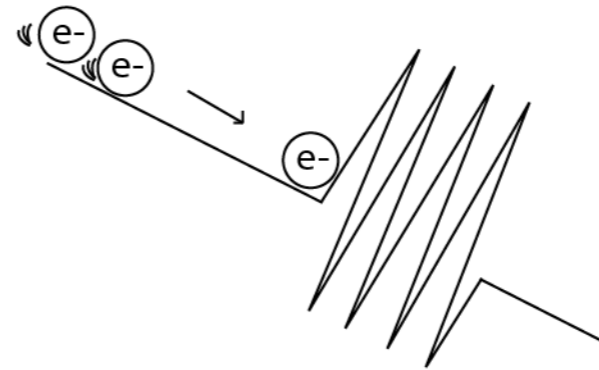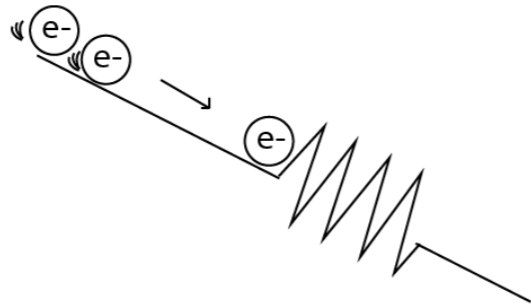
3) Slope + Obstacle = Motion with control






The simplest circuit

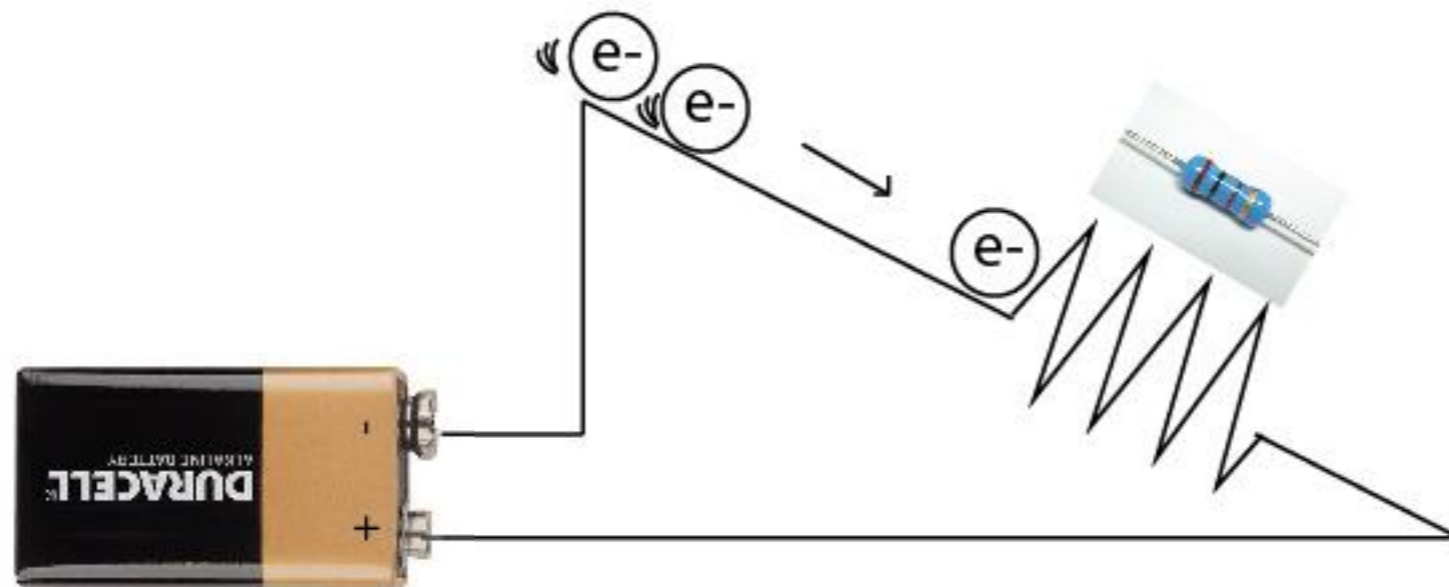

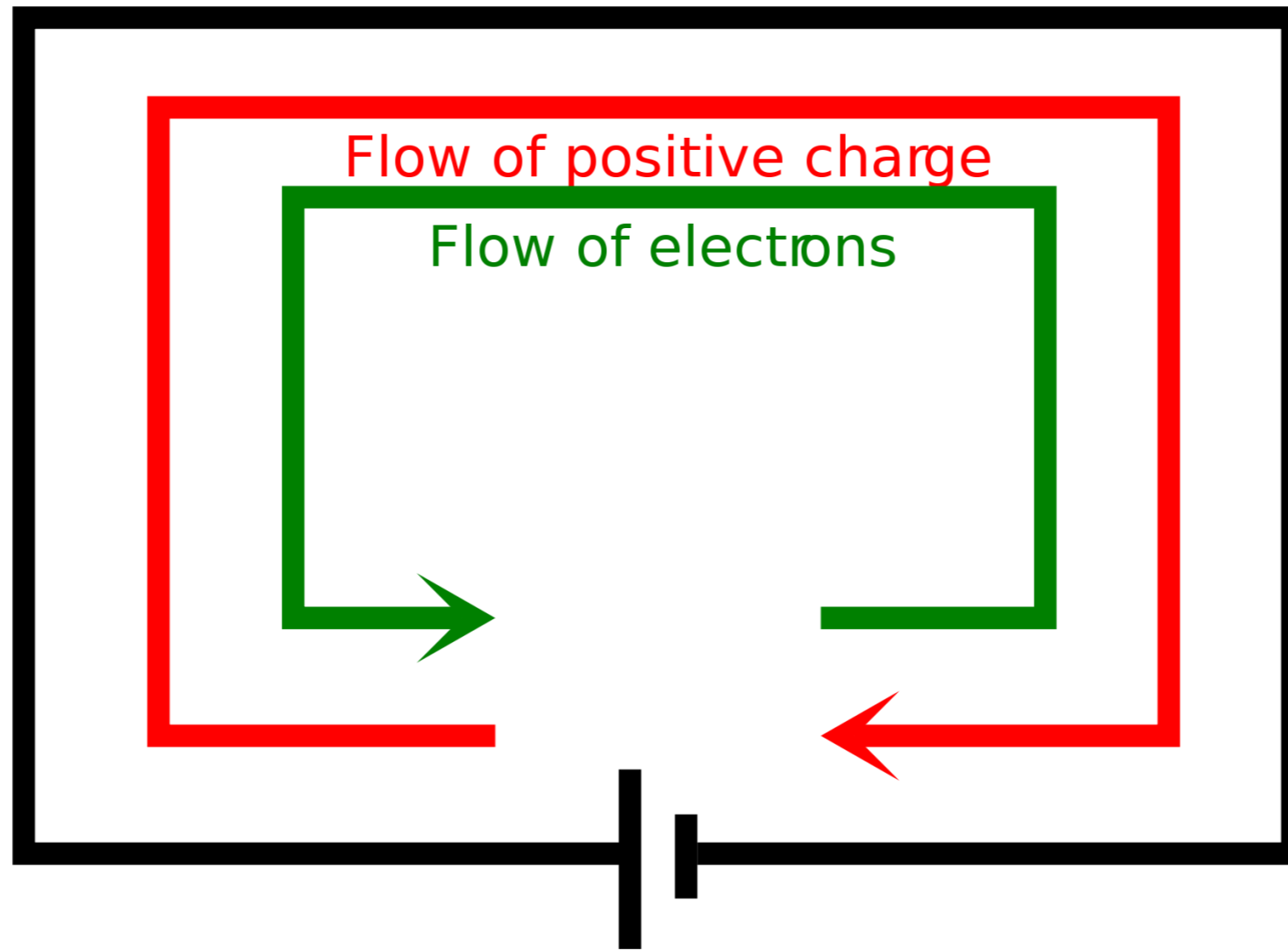



The simplest circuit – OHM'S LAW

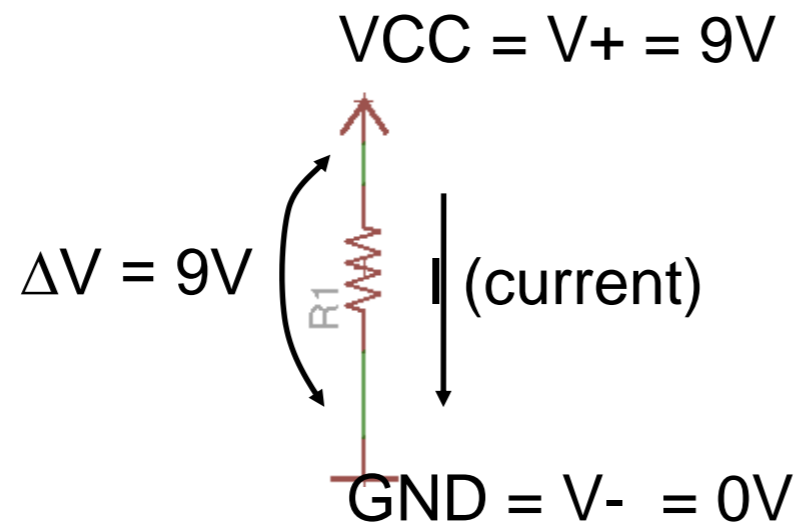

Ohm's Law

$$\Delta V = (V+) - (V-) = R \cdot I$$

$$V = RI$$

$$V = RI \Rightarrow I = V/R$$

$$R = V/I$$

Ex 1: Calculate Current you need

$$V = 9V$$

$$R1 = 1k\Omega = 1000\Omega$$

$$\rightarrow I = V/R = (VCC - GND) / I = (9V - 0V)/1000\Omega = 0.009 A (= 9 mA)$$

Ex 2: Calculate Resistor you need


$$V = 3V$$

$$I = 20mA$$

$$\rightarrow R = V/I = 3V/20mA = 3V/0.02A = 150\Omega$$



The simplest circuit - POWER

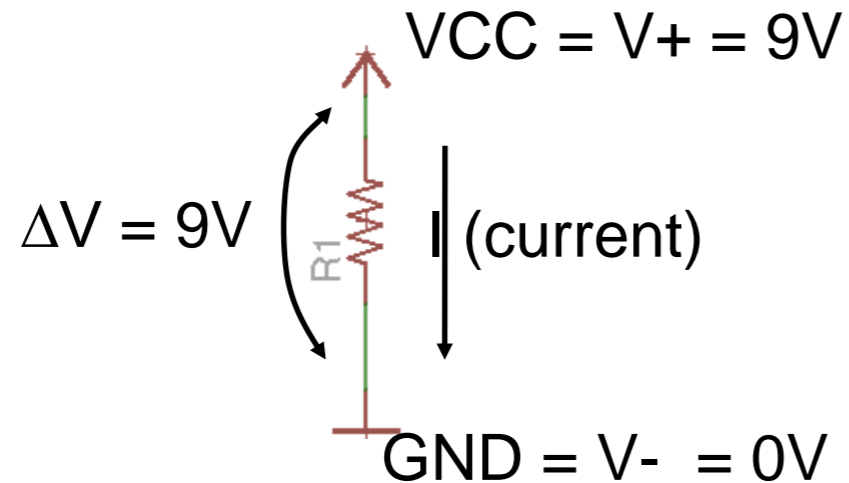

Power

Unit of measurement: Watt (W)

$$P = VI$$

$$V = RI \Rightarrow P = (R \cdot I) \cdot I = R \cdot I^2$$

When the power is higher than the power specified in the specs of the component:
The device burns.

Ex:


$$P = 9 \text{ V} \cdot 0.05 \text{ A} = 0.45 \text{ W}$$

$$(I = 5 \text{ mA} \Rightarrow R = 9 \text{ V} / 0.005 \text{ A} = 1800 \Omega = 1.8 \text{ k}\Omega)$$



Datasheets	Chip Resistor Marking RC Series, L Suffix Datasheet
Product Photos	1206 Chip Resistor, SMT
Product Training Modules	Chip Resistor
PCN Other	RC/AC 0603/0805/1206 22/Jan/2013
Standard Package ?	1
Category	Resistors
Family	Chip Resistor - Surface Mount
Series	RC1206
Packaging ?	Cut Tape (CT) ?
Resistance (Ohms)	10k
Tolerance	±1%
Power (Watts)	0.25W, 1/4W
Composition	Thick Film
Features	Moisture Resistant



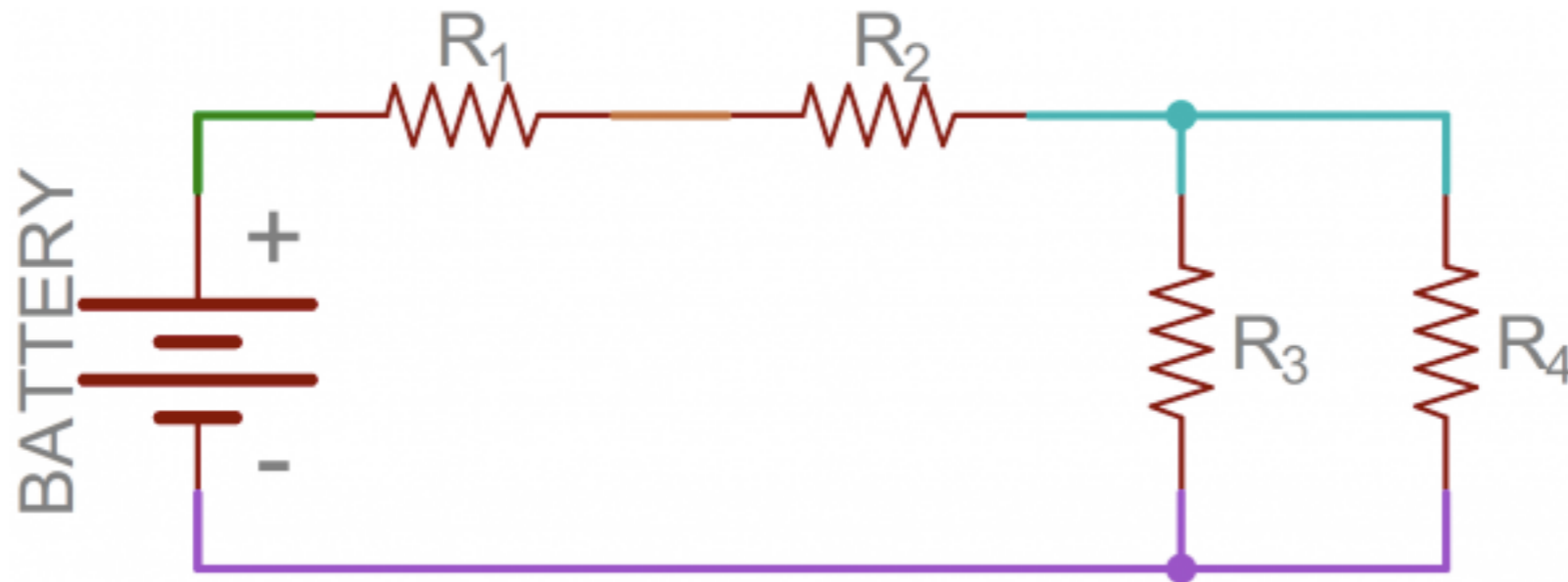The simplest circuit Plus – KIRCHHOFF'S LAW




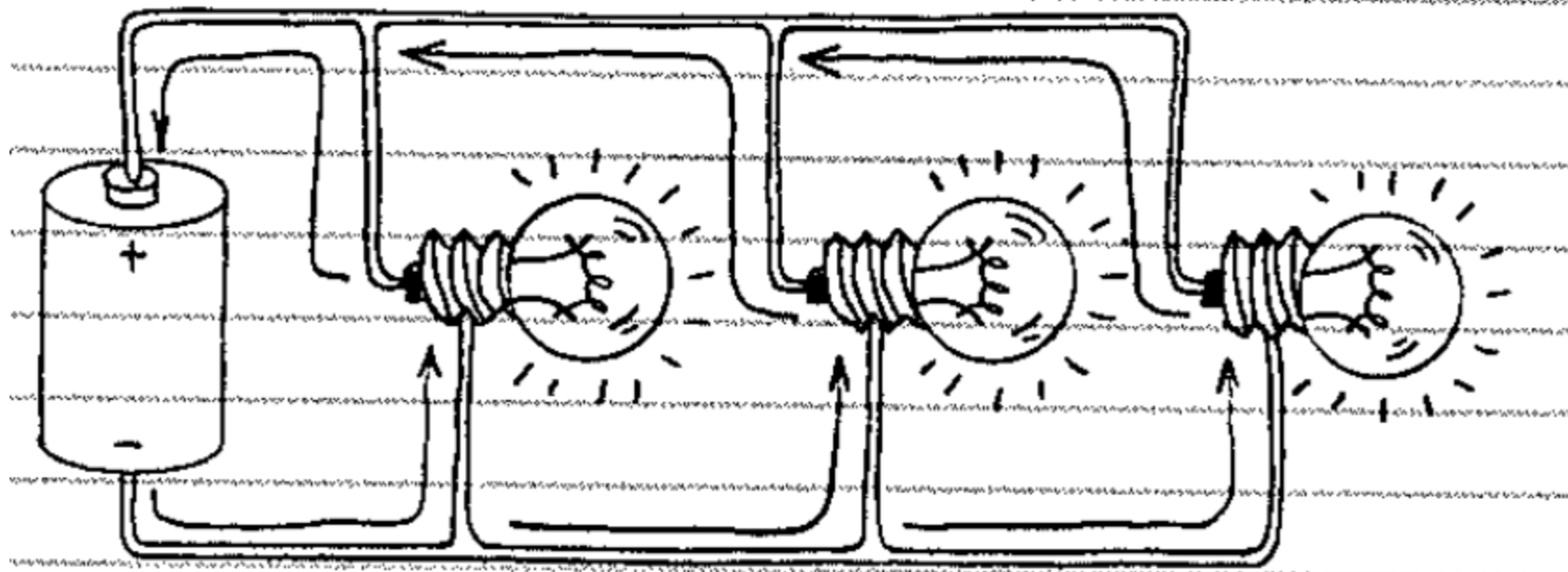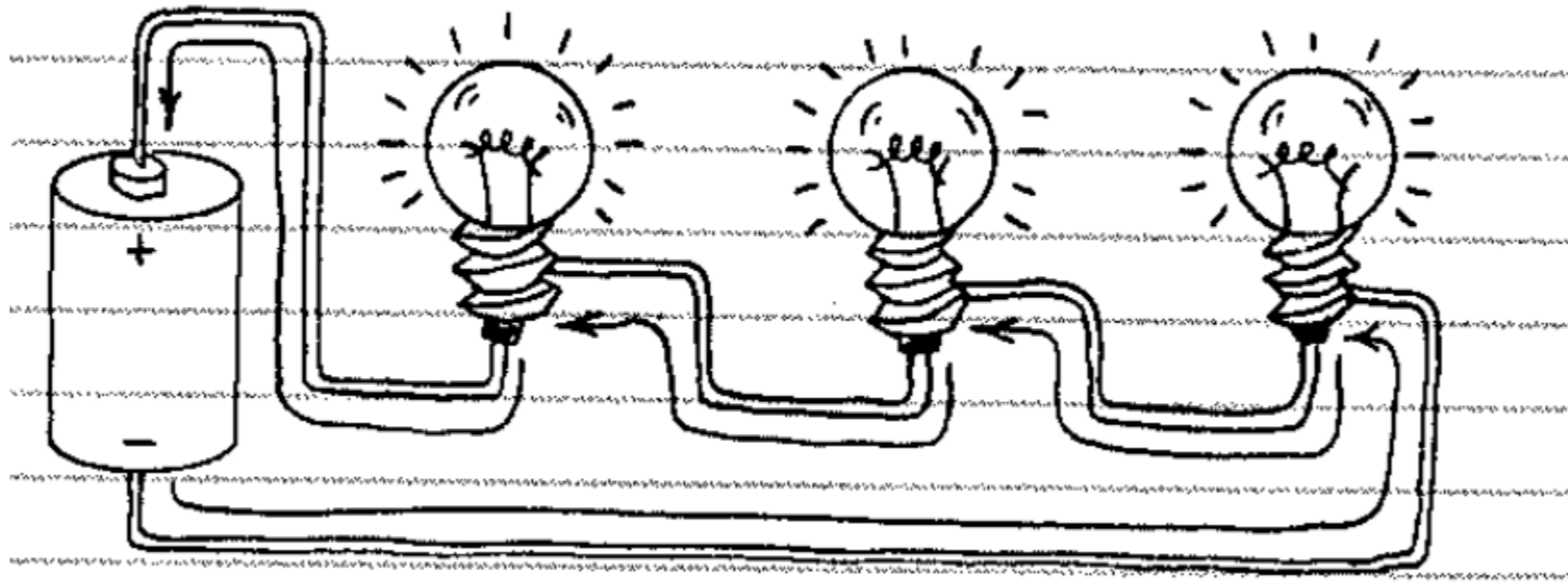
Example schematic with four uniquely colored nodes.






In Series – In Parallel

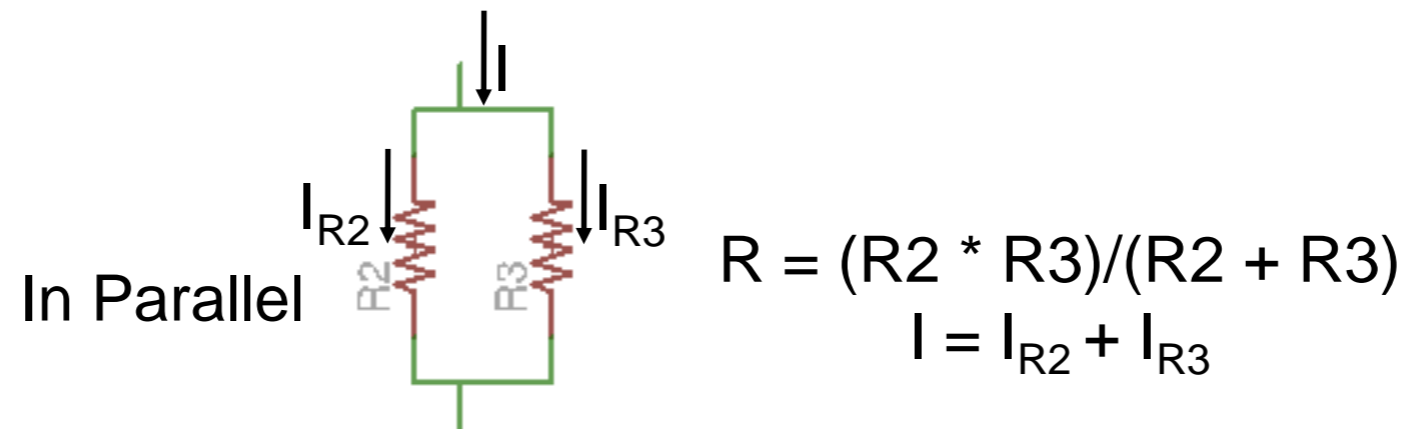

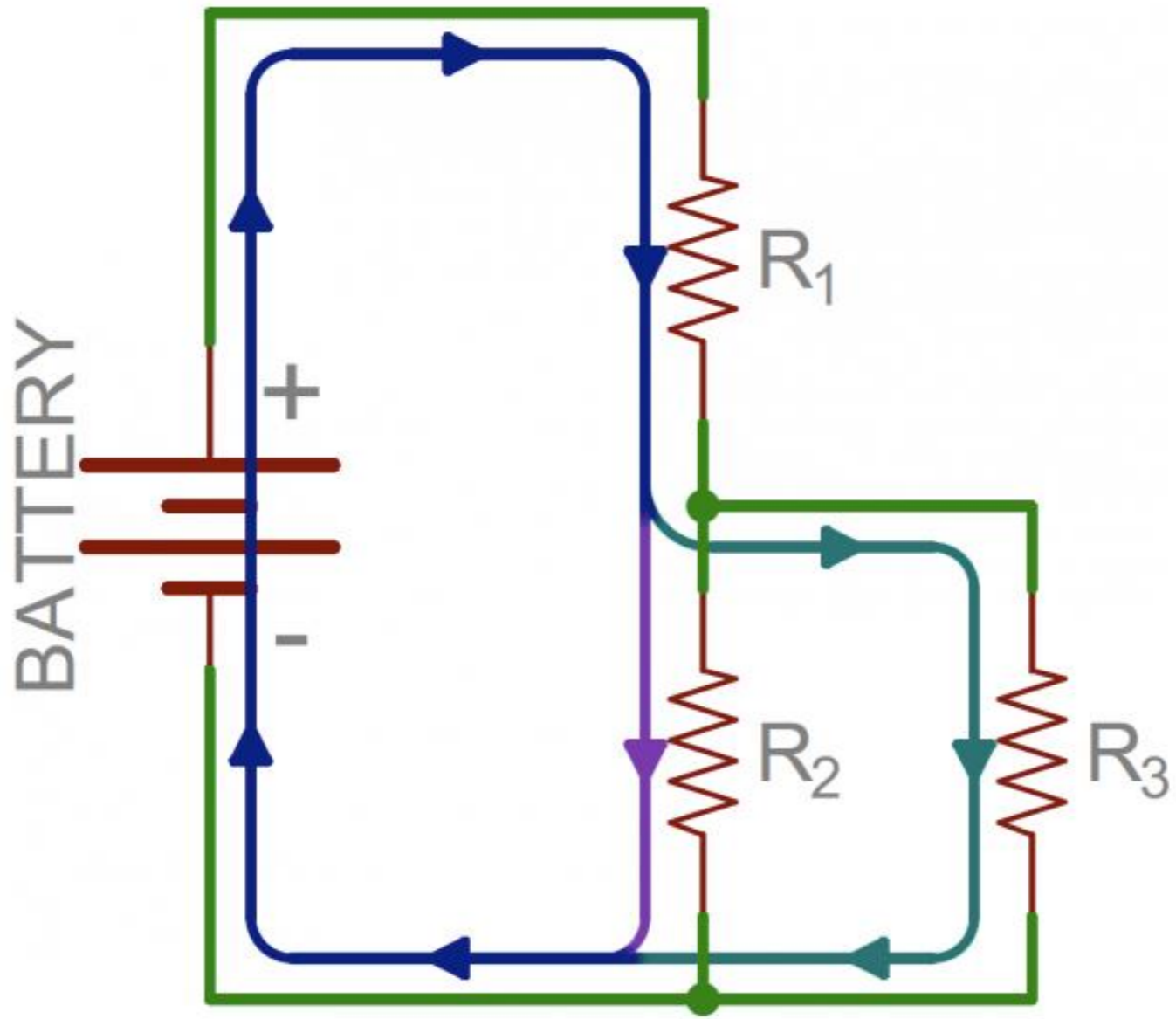





In Series – In Parallel

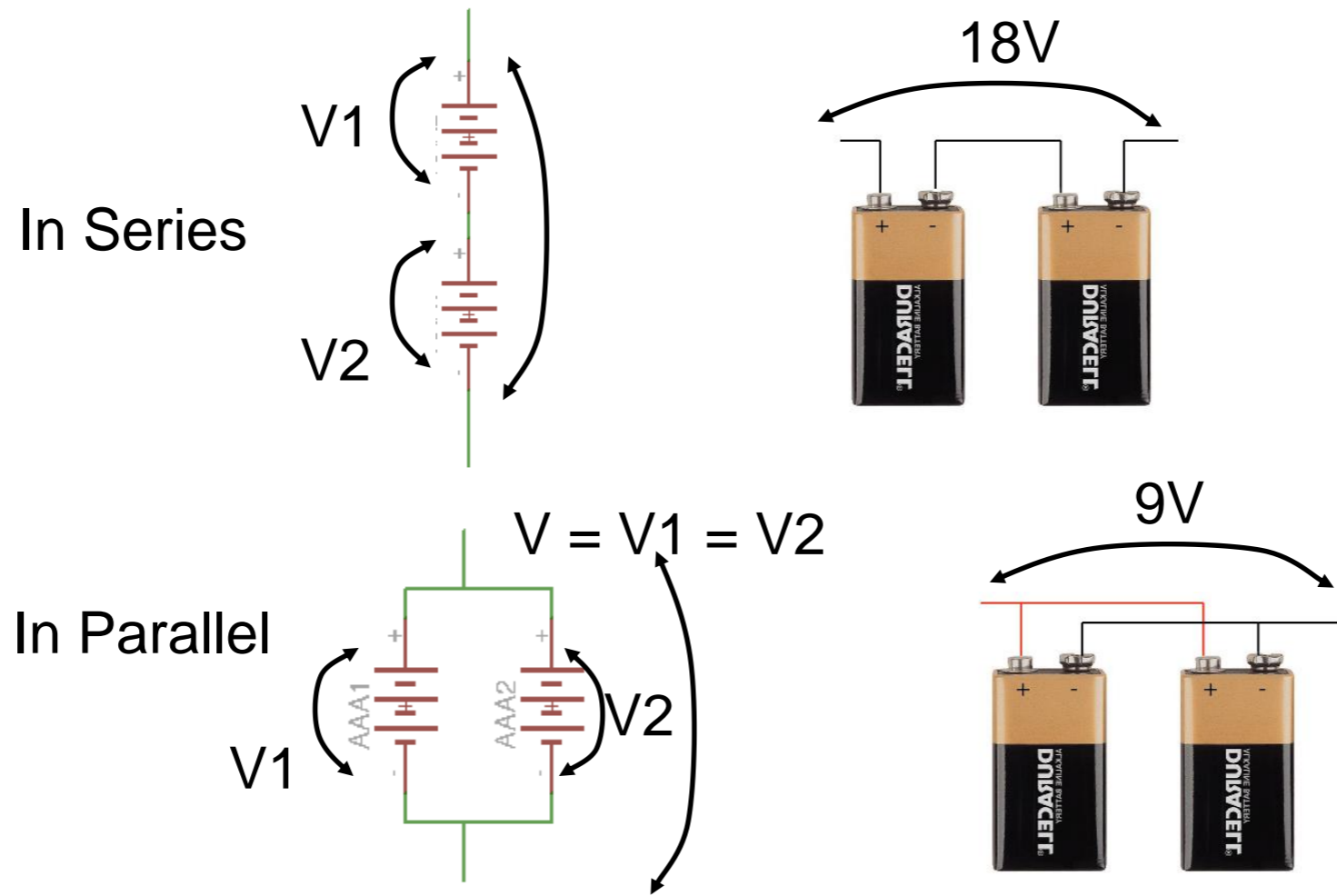





The simplest circuit + Switch

Tact Switch

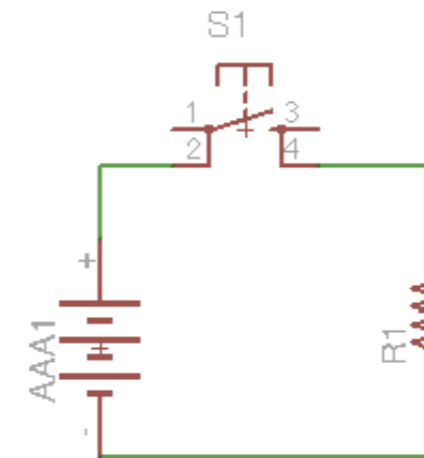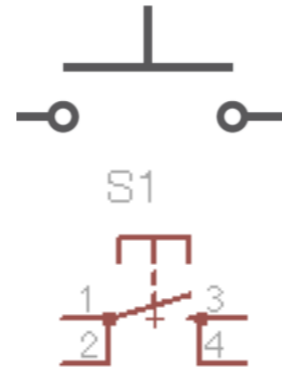




Slide Switch

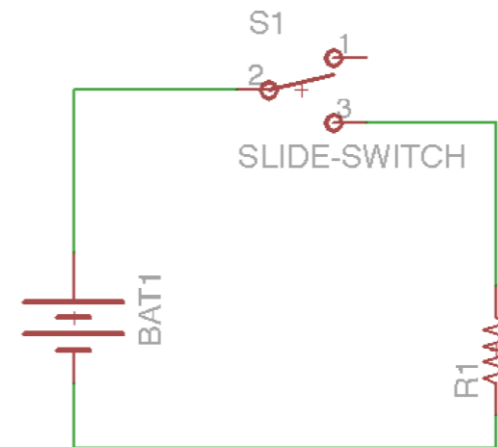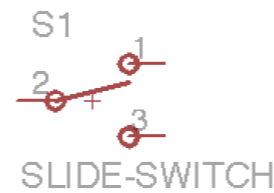


Note: place the switch to the high Voltage



The simplest circuit + LED

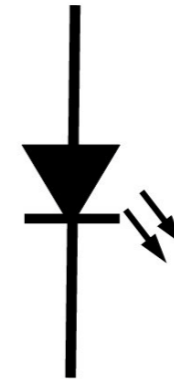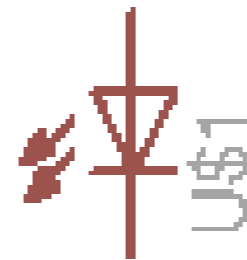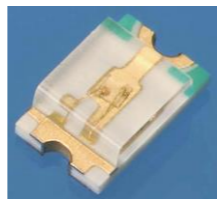

Anode (+)

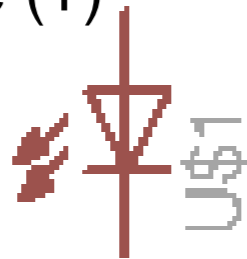

Cathode (-)

Ohm's Law doesn't work!

Forward Voltage (V_f)

Is the voltage at the sides of the LED when there is current through it.

Forward Current (I_f)


It's the maximum current that you fix.

Voltage - Forward (V_f) (Typ)	1.8V
Current - Test	10mA



RGB LED



Three LEDs in one

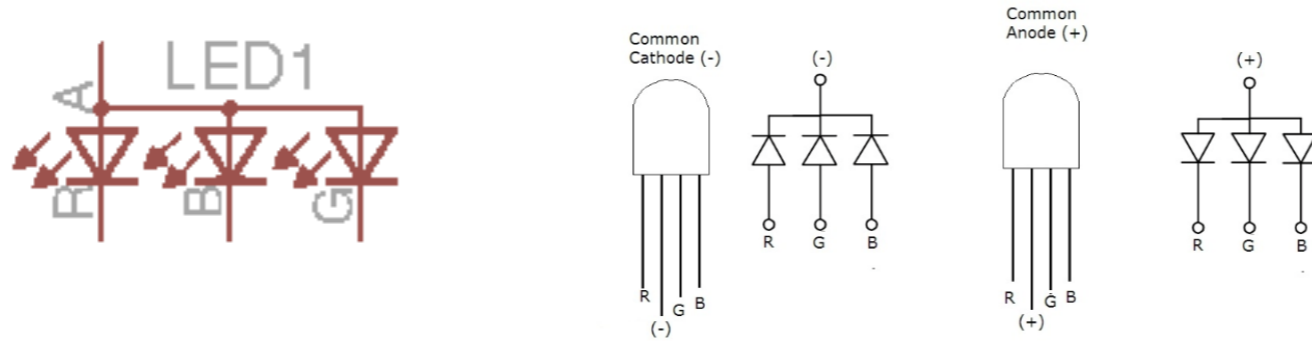



Components – Capacitor

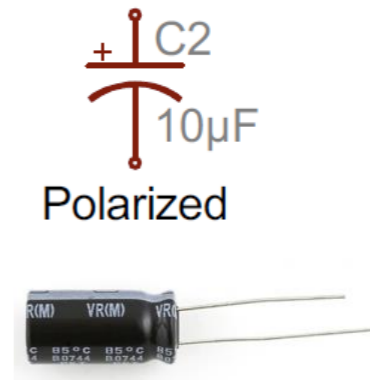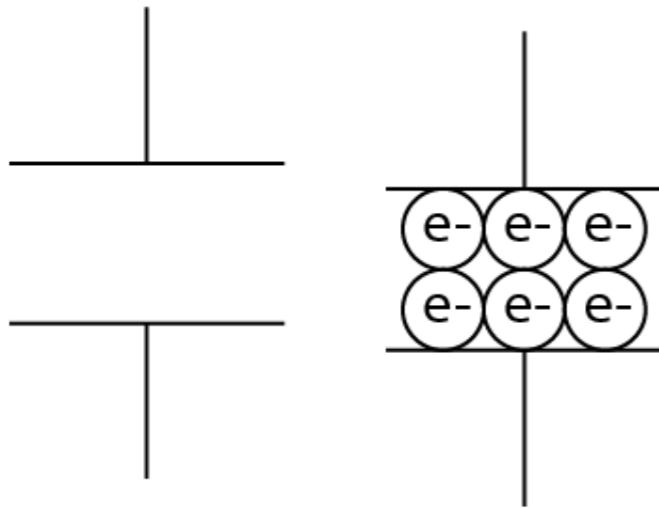Capacitor: energy storage. The current doesn't flow through the capacitor.





Prefix Name	Abbreviation	Weight	Equivalent Farads
Picofarad	pF	10^{-12}	0.000000000001 F
Nanofarad	nF	10^{-9}	0.000000001 F
Microfarad	μ F	10^{-6}	0.000001 F
Milifarad	mF	10^{-3}	0.001 F
Kilofarad	kF	10^3	1000 F




Components - Diode



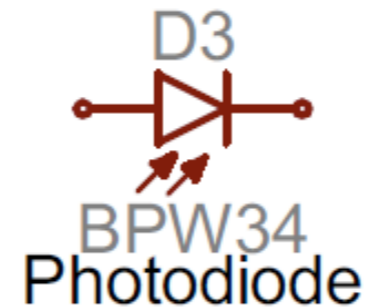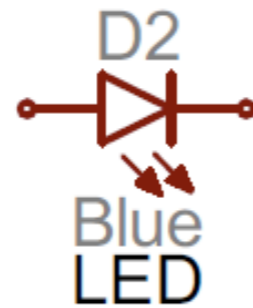ifferent **types of diodes**, each of which has a special riff on the standard symbol. **Photodiodes** (used in cameras, tiny solar cells), flip the arrows around and point them toward the diode.



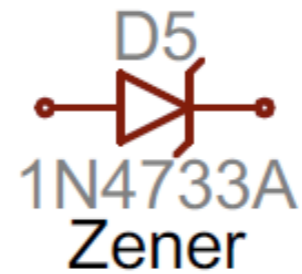
Diodes, like Schottky's or zeners, have their own symbols, with slight variations.





Schematic

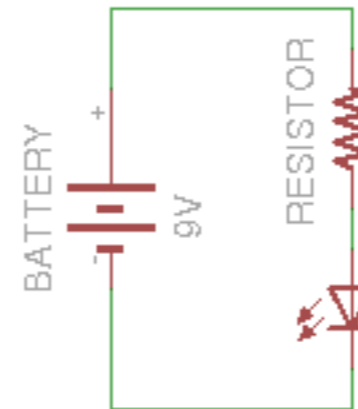The schematic is the symbolic representation of a circuit






How to read a Schematic

Names: Component names are usually a combination of one or two letters and a number. Ex: R1, R2.

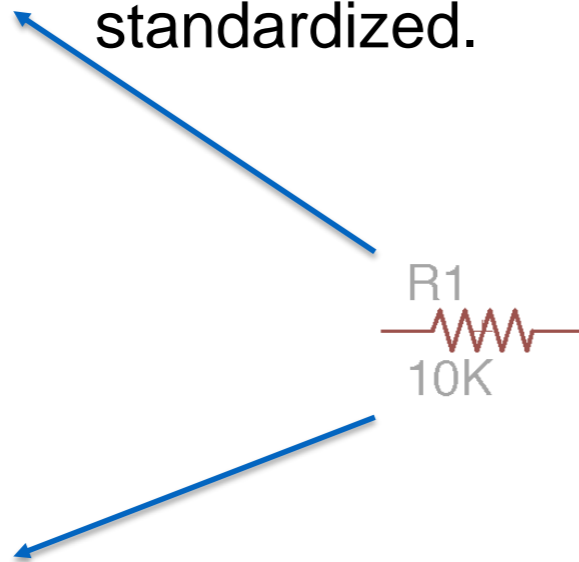The prefixes of names are pretty well standardized.



Values: help define exactly what a component is.

Name Identifier	Component
R	Resistors
C	Capacitors
L	Inductors
S	Switches
D	Diodes
Q	Transistors
U	Integrated Circuits
Y	Crystals and Oscillators





How to read a Schematic – Voltage Nodes





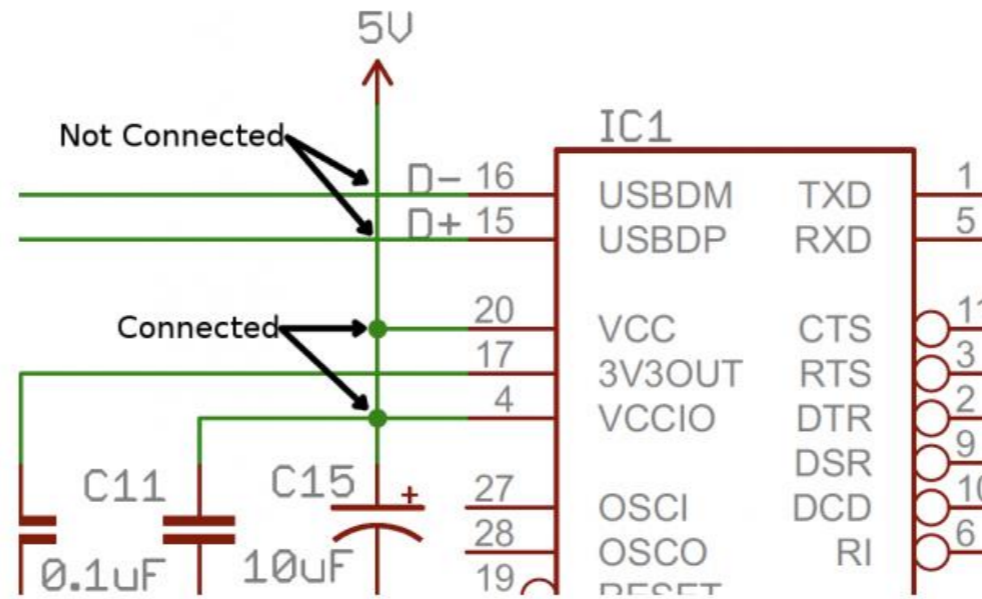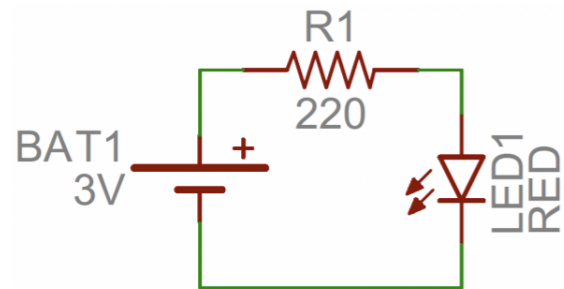How to read a Schematic – Nets & Junctions





Tinkering Time



some

rights

reserved